

Codefast - 6

1. Ideal Read.

For Ideal Case, Row 1 & Col 1 are grounded.

$$I_{col0} = (V_{row0} - V_{col0}) / R[0][0]$$
$$= (1V - 0V) / 1k\Omega = 1mA$$

2. Sneak Path Read

Row 1 & Col 1 are floating.

$$V_{row1} = x \quad V_{row0} = 1V$$
$$V_{col1} = y \quad V_{col0} = 0V$$

KCL @ row 1

$$(x - 0) / 2k\Omega + (x - y) / 1k\Omega = 0$$

X/y by $2k\Omega$

$$x + 2x - 2y = 0$$
$$3x - 2y = 0$$
$$y = 1.5x$$

KCL @ col 1

$$(y - 1) / 2k\Omega + (y - x) / 1k\Omega = 0$$

X/y by $2k\Omega$

$$y - 1 + 2y - 2x = 0$$
$$3y - 2x = 1$$

Sub $y = 1.5x$

$$\Rightarrow 3(1.5)x - 2x = 1$$
$$2.5x = 1$$
$$x = 0.4V$$

$$V_{row1} = 0.4V$$

$$V_{col1} = 0.6V$$

3. Actual I_{col0} including Sneak path

Current through intended path $R[0][0]$

$$I_{intended} = (1V - 0V) / 1k\Omega = 1mA$$

Sneak path current entering col0 through $R[1][0]$:

$$I_{sneak} = (V_{row1} - V_{col0}) / R[1][0]$$
$$= (0.4V - 0V) / 2k\Omega = 0.2mA$$

Total Sensed Column Current,

$$I_{col0_actual} = I_{intended} + I_{sneak}$$
$$= 1mA + 0.2mA$$
$$= 1.2mA$$

$$Actual I_{col0} = 1.2mA$$

4. Explanation.

The ideal MM result expects only the current from the selected cell $R[0][0]$, which is $1mA$. However, because row 1 & col 1 are floating, an additional sneak path current of $0.2mA$ flows into col0, increasing the sensed current to $1.2mA$.

This corrupts the MM result because the column current no longer represents only the intended dot product contribution

In large crossbar arrays, many such sneak paths can exist, causing read errors & making accurate sensing more difficult.